



Roll No: 20PH20014

Name: Jessica John Britto

Date: 27/08/2021

ELECTROMAGNETISM LABORATORY

EXPERIMENT-1

Aim:

1. To study the current-voltage relationship in an ac circuit containing an inductor and an external resistor in series.
2. To study the variation of the resistance of the inductor with the frequency of the ac source and hence to determine the inductance.
3. To draw the phasor diagram and hence to determine the inductance and the resistance of the inductor.

Theory:

In figure. 3.EM14(i), a series combination of an external resistance R and an inductor (coil) of inductance L and resistance r is connected to an ac source of angular frequency ω and RMS voltage V . If I is the RMS current flowing in the circuit and V_R is the RMS voltage across the resistance R , then

$$I = \frac{V_R}{R} \quad \dots (i)$$

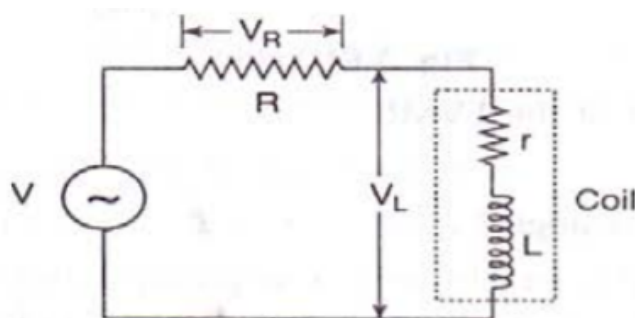


Fig. 3.EM14(i)

If V_L is the RMS voltage across the inductor, then $V_L = \sqrt{r^2 + X_L^2} \cdot I \rightarrow (ii)$ Where X_L is the inductive resistance: $X_L = \omega L = 2\pi f L \rightarrow (iii)$, f being the frequency in Hz. The resistance r accounts for the losses in the inductor. The impedance of the inductor is

$$Z_L = \frac{V_L}{I} = \sqrt{r^2 + X_L^2} \rightarrow (iv)$$

1. The current I can be determined from Eq. (i) by measuring the voltage V_R and knowing the resistance R . If the voltage V_L across the inductor is also measured, then at a given frequency $V_L \propto I$. Thus the plot of V_L along the x-axis and I along the y-axis will be a straight line passing through the origin [vide Eq.(ii)]. This shows that the current-voltage relationship in an ac circuit containing an inductor obeys Ohm's law. The slope of the $V_L - I$ plot gives $1/Z_L$. Let Z_1 and Z_2 be the values of Z_L for two frequencies $f_1 (= \omega_1 / 2\pi)$ and $f_2 (= \omega_2 / 2\pi)$. Then $Z_1^2 = r^2 + \omega_1^2 L^2$ and $Z_2^2 = r^2 + \omega_2^2 L^2$. These two equations give

$$L = \frac{1}{2\pi} \cdot \sqrt{\frac{Z_2^2 - Z_1^2}{f_2^2 - f_1^2}} \rightarrow (v)$$

and

$$r = \sqrt{\frac{Z_1^2 f_2^2 - Z_2^2 f_1^2}{f_2^2 - f_1^2}} \quad \dots (vi)$$

[The quantity $Z_1^2 f_2^2 - Z_2^2 f_1^2$ is quite small, and can turn out to be negative due to experimental errors. In that case, r cannot be found from Eq. (vi).]

- By measuring V_R and V_L at different frequencies, Z_L can be calculated from Eqs. (i) and (iv) at those frequencies. If Z_L (along the y-axis) is plotted against f (along the x-axis), we get the graph of Fig. 3.EM14(ii). The intercept of the curve on the Z_L -axis gives the resistance r . At high frequencies, $X_L \gg r$, so that $Z_L = X_L$. Hence the graph at high frequencies is almost linear, the slope of which is $2\pi L$. Thus from the slope, the inductance L can be found.

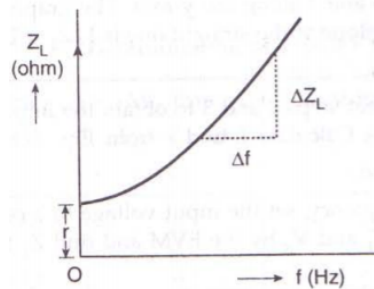


Fig. 3.EM14(ii)

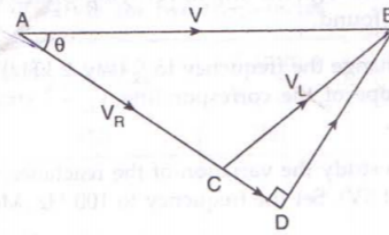


Fig. 3.EM14(iii)

- The phasor diagram for the voltages is shown in Fig. 3.EM14(iii). The phasors V , V_R and V_L are represented (with a proper choice of scale) by the sides AB , AC , and CB of the triangle ABC . If BD is perpendicular to AC (extended), CD and DB give the phasors Ir and IX_L respectively. Since AC gives the phasor IR , we have

$$\frac{AC}{DB} = \frac{IR}{IX_L} = \frac{R}{2\pi fL}$$

Hence the inductance

$$L = \frac{R}{2\pi f} \cdot \frac{DB}{AC}$$

Again

$$\frac{AC}{CD} = \frac{IR}{Ir} = \frac{R}{r}$$

So that

$$r = R \cdot \frac{CD}{AC}$$

The phase angle θ by which the current I lags the source voltage V is given by $\theta = \arctan \left(\frac{DB}{AD} \right)$. So, L , r and θ can be found from the phasor diagram using Eqs. (vii), (viii) and (ix), respectively.

Apparatus and Accessories:

- An air-core coil ($L = 30 \text{ mH}$, $r = 50\Omega$)
- Some carbon resistors or a resistance box ($0-1000\Omega$)
- An audio oscillator of low output impedance
- An electronic voltmeter (EVM)

Experimental Results:

TABLE-01

$$V_R - V_L (DATA); R = 47\Omega$$

Frequency of ac source $f = 1 \text{ kHz} = f_1$; Least count of the voltmeter is $\Delta V = 0.001 \text{ V}$ and least count of function generator $\Delta f = 0.1 \text{ Hz}$

| S. No. | Input voltage peak to peak V_{pp} (V) | Input voltage in r.m.s V_{rms} (Volts) | Voltage across R, V_R (r.m.s) (Volts) | Voltage across L, V_L (r.m.s) (Volts) | $I = \frac{V_R}{R}$ (amp) |
|--------|---|--|---|---|---------------------------|
| 01 | 0.5 | 0.177 | 0.046 | 0.131 | 0.0009787234043 |
| 02 | 1.0 | 0.353 | 0.086 | 0.270 | 0.001829787234 |
| 03 | 1.5 | 0.530 | 0.104 | 0.426 | 0.002212765957 |
| 04 | 2.0 | 0.707 | 0.124 | 0.580 | 0.002638297872 |
| 05 | 2.5 | 0.883 | 0.150 | 0.734 | 0.003191489362 |
| 06 | 3.0 | 1.060 | 0.176 | 0.888 | 0.003744680851 |
| 07 | 3.5 | 1.237 | 0.204 | 1.038 | 0.004340425532 |
| 08 | 4.0 | 1.414 | 0.225 | 1.192 | 0.004787234043 |
| 9 | 4.5 | 1.590 | 0.244 | 1.346 | 0.005191489362 |
| 10 | 5.0 | 1.767 | 0.267 | 1.500 | 0.005680851064 |

TABLE-02

$$V_R - V_L (DATA); R = 47\Omega$$

Frequency of ac source, $f = 2 \text{ kHz} = f_1$; Least count of the voltmeter is $\Delta V = 0.001 \text{ V}$ and least count of function generator $\Delta f = 0.01 \text{ Hz}$

| S. No. | Input voltage peak to peak V_{pp} (V) | Input voltage in r.m.s V_{rms} (Volts) | Voltage across R, V_R (r.m.s) (Volts) | Voltage across L, V_L (r.m.s) (Volts) | $I = \frac{V_R}{R}$ (amp) |
|--------|---|--|---|---|---------------------------|
| 01 | 0.5 | 0.177 | 0.025 | 0.146 | 0.0005319148936 |
| 02 | 1.0 | 0.353 | 0.048 | 0.298 | 0.001021276596 |
| 03 | 1.5 | 0.530 | 0.071 | 0.458 | 0.001510638298 |
| 04 | 2.0 | 0.707 | 0.094 | 0.612 | 0.002 |
| 05 | 2.5 | 0.883 | 0.116 | 0.765 | 0.002468085106 |
| 06 | 3.0 | 1.060 | 0.138 | 0.926 | 0.002936170213 |
| 07 | 3.5 | 1.237 | 0.160 | 1.128 | 0.003404255319 |
| 08 | 4.0 | 1.414 | 0.183 | 1.225 | 0.003893617021 |
| 9 | 4.5 | 1.590 | 0.205 | 1.384 | 0.004361702128 |

| | | | | | |
|----|-----|-------|-------|-------|---------------|
| 10 | 5.0 | 1.767 | 0.221 | 1.547 | 0.00470212766 |
|----|-----|-------|-------|-------|---------------|

TABLE-03

Determination of L and r from V_L -I curves for two frequencies

| Frequencies f (Hz) | ΔV_L from V_L -I plot (V) | ΔI from V_L -I plot (A) | $Z_L = \frac{\Delta V_L}{\Delta I} \Omega$ | L from Eq. (v) (H) | r from Eq. (vi)* (Ω) |
|------------------------|--|--------------------------------------|--|-----------------------|----------------------------------|
| 1 k (=f ₁) | 0.612 | 0.00214893617 | 284.7920792 | 0.0149512932 | 268.8687828 |
| 2k (=f ₃) | 0.628 | 0.001914893617 | 327.9555556 | | |

*r cannot be found from Eq. (vi) if $Z_1^2 f_2^2 - Z_2^2 f_1^2$ turns out to be negative due to experimental errors.

TABLE-04

Variation of ZL with frequency

Given R = 47 Ω and applied input voltage peak to peak V_{pp} = 5 volts i.e. V_{rms} = 1.768 volts

| Frequencies f (Hz) | V_R (r.m.s) (Volts) | V_L (r.m.s) (Volts) | $I = \frac{V_R}{R}$ (amp) | $Z_L = \frac{V_L}{I} \Omega$ |
|-----------------------|--------------------------|--------------------------|---------------------------|------------------------------|
| 100 | 1.196 | 0.570 | 0.02544680851 | 22.39966555 |
| 200 | 0.909 | 0.857 | 0.01934042553 | 44.31133113 |
| 300 | 0.745 | 1.025 | 0.01585106383 | 64.66442953 |
| 400 | 0.638 | 1.132 | 0.01357446809 | 83.39184953 |
| 500 | 0.562 | 1.205 | 0.01195744681 | 100.7740214 |
| 600 | 0.504 | 1.267 | 0.01072340426 | 118.1527778 |
| 700 | 0.459 | 1.310 | 0.009765957447 | 134.1394336 |
| 800 | 0.422 | 1.343 | 0.008978723404 | 149.5758294 |
| 900 | 0.390 | 1.379 | 0.00829787234 | 166.1871795 |
| 1000 | 0.364 | 1.408 | 0.007744680851 | 181.8021978 |
| 1100 | 0.340 | 1.424 | 0.007234042553 | 196.8470588 |
| 1200 | 0.320 | 1.450 | 0.006808510638 | 212.96875 |
| 1300 | 0.298 | 1.471 | 0.006340425532 | 232.0033557 |
| 1400 | 0.289 | 1.478 | 0.00614893617 | 240.366782 |
| 1500 | 0.276 | 1.491 | 0.005872340426 | 253.9021739 |
| 1600 | 0.263 | 1.501 | 0.005595744681 | 268.2395437 |

| | | | | |
|------|-------|-------|----------------|-------------|
| 1700 | 0.250 | 1.517 | 0.005319148936 | 285.196 |
| 1800 | 0.240 | 1.529 | 0.005106382979 | 299.4291667 |
| 1900 | 0.232 | 1.531 | 0.004936170213 | 310.1594828 |
| 2000 | 0.222 | 1.547 | 0.004723404255 | 327.518018 |
| 2100 | 0.214 | 1.552 | 0.004553191489 | 340.8598131 |
| 2200 | 0.206 | 1.561 | 0.004382978723 | 356.1504854 |
| 2300 | 0.200 | 1.566 | 0.004255319149 | 368.01 |
| 2400 | 0.193 | 1.574 | 0.004106382979 | 383.3056995 |
| 2500 | 0.187 | 1.583 | 0.003978723404 | 397.8663102 |
| 2600 | 0.181 | 1.589 | 0.00385106383 | 412.6132597 |
| 2700 | 0.176 | 1.594 | 0.003744680851 | 425.6704545 |
| 2800 | 0.170 | 1.600 | 0.003617021277 | 442.3529412 |
| 2900 | 0.166 | 1.604 | 0.003531914894 | 454.1445783 |
| 3000 | 0.161 | 1.607 | 0.003425531915 | 469.1242236 |
| 3100 | 0.157 | 1.611 | 0.003340425532 | 482.2738854 |
| 3200 | 0.153 | 1.615 | 0.003255319149 | 496.1111111 |
| 3300 | 0.149 | 1.619 | 0.003170212766 | 510.6912752 |
| 3400 | 0.145 | 1.623 | 0.003085106383 | 526.0758621 |
| 3500 | 0.142 | 1.626 | 0.003021276596 | 538.1830986 |
| 3600 | 0.138 | 1.630 | 0.002936170213 | 555.1449275 |
| 3700 | 0.135 | 1.633 | 0.002872340426 | 568.5259259 |
| 3800 | 0.131 | 1.637 | 0.002787234043 | 587.3206107 |
| 3900 | 0.128 | 1.640 | 0.002723404255 | 602.1875 |
| 4000 | 0.126 | 1.642 | 0.002680851064 | 612.4920635 |
| 4100 | 0.123 | 1.645 | 0.002617021277 | 628.5772358 |
| 4200 | 0.120 | 1.648 | 0.002553191489 | 645.4666667 |
| 4300 | 0.118 | 1.650 | 0.002510638298 | 657.2033898 |
| 4400 | 0.116 | 1.652 | 0.002468085106 | 669.3448276 |
| 4500 | 0.112 | 1.656 | 0.002382978723 | 694.9285714 |
| 4600 | 0.110 | 1.658 | 0.002340425532 | 708.4181818 |
| 4700 | 0.108 | 1.660 | 0.00229787234 | 722.4074074 |
| 4800 | 0.106 | 1.662 | 0.002255319149 | 736.9245283 |
| 4900 | 0.104 | 1.664 | 0.002212765957 | 752 |
| 5000 | 0.102 | 1.666 | 0.002170212766 | 767.6666667 |
| | | | | |

TABLE-05

Determination of L and r from Z_L -f plot for any three frequencies

| From the straight portion of the curve | | | Intercept on the Z_L axis = r (Ω) |
|--|-----------------|--|--|
| ΔZ_L (Ω) | Δf (Hz) | $L = \frac{1}{2\pi} \cdot \frac{\Delta Z_L}{\Delta f} (H)$ | |
| 145.7158202 | 1000 | 0.023191393 | 29 |

TABLE-06

Given $R = 47 \Omega$ and applied input voltage peak to peak $V_{pp} = 5$ volts i.e. $V_{rms} = 1.768$ volts

Least count of voltmeter is $\Delta V = 0.001 V$ and least count of function generator $\Delta f = 0.1 Hz$

| S. No. | Frequency f (Hz) | Input voltage in r.m.s V_{rms} (Volts) | Voltage across R, V_R (r.m.s) (Volts) | Voltage across L, V_L (r.m.s) (Volts) |
|--------|------------------|--|---|---|
| 01 | 1000 | 1.768 | 0.364 | 1.408 |
| 02 | 2000 | 1.768 | 0.222 | 1.547 |
| 03 | 3000 | 1.768 | 0.161 | 1.607 |
| 04 | 4000 | 1.768 | 0.126 | 1.642 |

Choose of the scale for the phasor diagram: 1 cm =0.1 Volts

| S. No. | Frequency f (Hz) | Input voltage AB ($\equiv V_{rms}$) (cm) | Voltage across R, AC ($\equiv V_R$) (cm) | Voltage across L, CB ($\equiv V_L$) (cm) |
|--------|------------------|--|--|--|
| 01 | 1000 | 17.68 | 3.64 | 14.08 |
| 02 | 2000 | 17.68 | 2.22 | 15.47 |
| 03 | 3000 | 17.68 | 1.61 | 16.07 |
| 04 | 4000 | 17.68 | 1.26 | 16.42 |

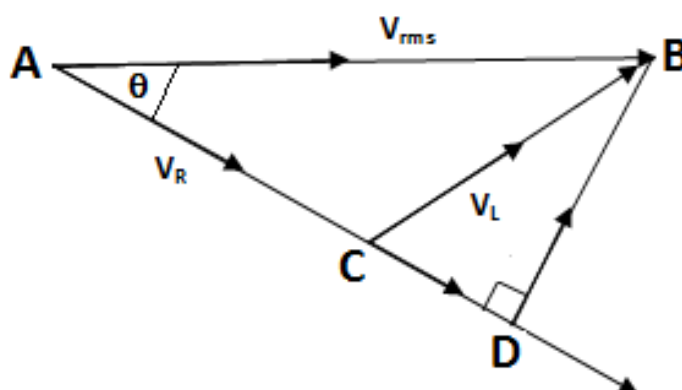


TABLE-07

Determination L, r and θ from phasor diagram:

$$R = 47 \Omega$$

| S. No. | f (Hz) | AC (cm) | DB (cm) | CD (cm) | L from Eq. (vii) (H) | r from Eq. (viii) (ohm) | θ from Eq. (ix) (degree s) |
|--------|--------|---------|-------------|-------------|----------------------|-------------------------|-----------------------------------|
| 01 | 1000 | 3.64 | 2.332261207 | 13.88549451 | 0.004795280532 | 179.2907258 | 7.580279984 |
| 02 | 2000 | 2.22 | 1.567928964 | 15.39033784 | 0.002642905453 | 325.8314767 | 5.087889579 |
| 03 | 3000 | 1.61 | 1.33 | 16.3 | 0.0021 | 475.84 | 4.31 |
| 04 | 4000 | 1.26 | 1.5 | 16.1 | 0.0022 | 601.12 | 4.9 |

Calculations:

L, r and θ can be determined from the following equations of the phasor diagram-


$$\frac{AC}{DB} = \frac{IR}{IX_L} = \frac{R}{2\pi fL}$$

DB can be found from this equation $\cos \theta = \frac{AB^2 + AC^2 - BC^2}{2 \cdot AB \cdot AC}$ and $DB = \sin \theta \cdot AB$

L can be found from this equation $L = \frac{R}{2\pi f} \cdot \frac{DB}{AC}$

CD can be found from this equation $\frac{AC}{CD} = \frac{IR}{Ir} = \frac{R}{r}$

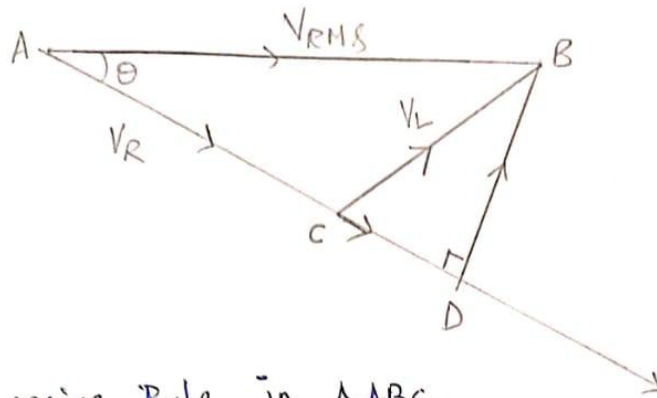r and θ can be found from the following equations $r = R \cdot \frac{CD}{AC}$ and $\theta = \arctan \left(\frac{DB}{AD} \right)$



Using cosine Rule in $\triangle ABC$,

$$\cos \theta = \frac{V_{RMS}^2 + V_R^2 - V_L^2}{2 V_{RMS} V_R} \quad \text{--- (1)} \quad \begin{aligned} |V_{RMS}| &= AB \\ |V_R| &= AC \\ |V_L| &= BC \end{aligned}$$

In $\triangle ABD$, $\sin \theta = \frac{DB}{AB}$

$$\Rightarrow DB = \sin \theta (AB)$$

\therefore , for set-1, $f = 1000 \text{ Hz}$, $AB = 17.68 \text{ cm}$, $AC = 3.64 \text{ cm}$,
 $BC = 14.08 \text{ cm}$

$$\cos \theta = \frac{(17.68)^2 + (3.64)^2 - (14.08)^2}{2 (17.68)(3.64)}$$

$$\theta = 7.5803^\circ$$

$$DB = \sin \theta (17.68) = 2.33 \text{ cm}$$

$$L = \frac{R}{2\pi f} \cdot \frac{DB}{AC} = \frac{47}{2\pi(1000)} \cdot \frac{(2.33)}{3.64}$$

$$L = 4.7882026 \times 10^{-3} \text{ H}$$

$$L = 0.0047882026 \text{ H}$$

From $\triangle BCD$, $BC^2 = CD^2 + BD^2$
 $CD^2 = BC^2 - BD^2$

$$CD = 13.8858 \text{ cm}$$

$$r = R \left(\frac{CD}{AC} \right) = 47 \times \frac{13.8858}{3.64} = 179.2956$$


$$\therefore, r = 179.2956273 \Omega$$

Similarly, the same process can be applied to the remaining sets to find L , r and θ

Graphs:


Plot of V_L vs I of Table-1:

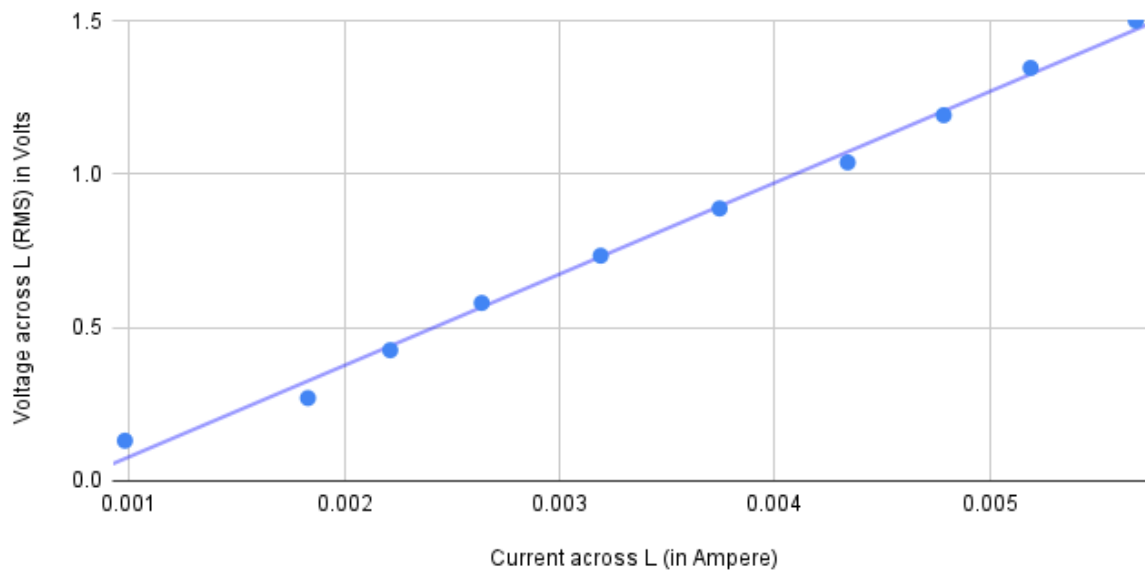Voltage across L (RMS) vs Current across L for $f = 1\text{ kHz}$




Plot of V_L vs I of Table-2:

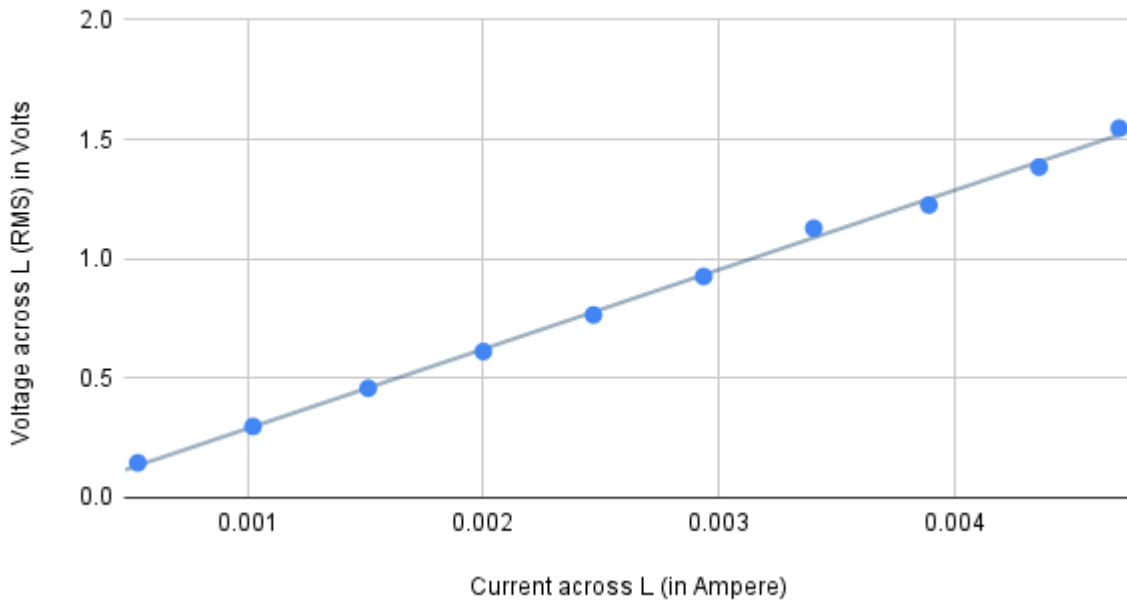Voltage across L(RMS) vs Current across L for f =2k Hz



Plot of Z_L vs f of Table-5:

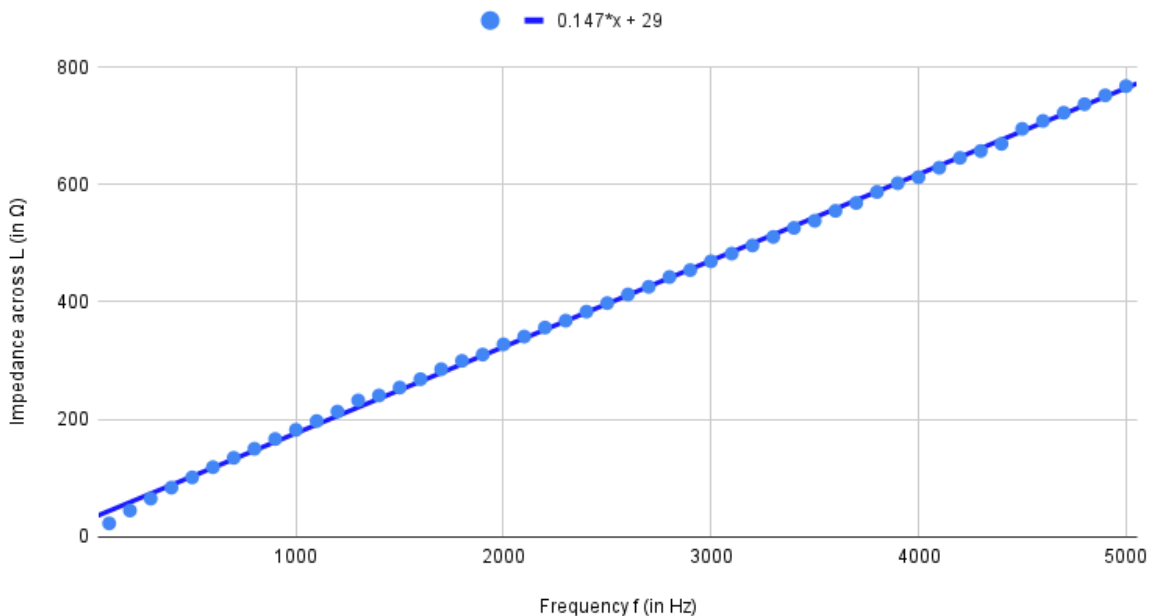Impedance across L (in Ω) vs frequency (in Hz)



Equation of the graph when Z_L vs f of Table-5 is plotted - $Z_L = 0.147 \cdot f + 29$

Proportional error in L:

We have $V_L = 2\pi f L I = 2\pi f L \frac{V_R}{R}$

$$L = \frac{R}{2\pi f} \cdot \frac{V_L}{V_R}$$

or ,

Since R is given, there will be no error due to R, hence the proportional error in L is

$$\frac{\delta L}{L} = \frac{\delta f}{f} + \frac{\delta V_R}{V_R} + \frac{\delta V_L}{V_L},$$

Where δf , δV_R and δV_L are the errors in f , V_R , and V_L respectively; these errors correspond to the smallest scale divisions of the respective measuring instruments.

Substituting the values of $\frac{\delta f}{f}$, $\frac{\delta V_R}{R}$, and $\frac{\delta V_L}{L}$ for a particular measurement, the proportional error $\frac{\delta L}{L}$ can be calculated.

Calculations-

For $f = 2k\text{ Hz}$, $V_R = 0.116\text{ V}$, $V_L = 0.765\text{ V}$, $\delta V = 0.001\text{ V}$, $\delta f = 0.01\text{ Hz}$, the proportional error in L is-

$$\frac{\delta L}{L} = \frac{0.01}{2000} + \frac{0.001}{0.116} + \frac{0.001}{0.765}$$

Therefore, the proportional error $\frac{\delta L}{L}$ is 0.99%

Precautions and Discussion:

1. If the amplitude of the output voltage of the oscillator changes with the frequency it should be adjusted.
2. The resistance R must be noninductive.
3. The connecting wires should be straight and short.
4. Instead of an EVM, a CRO can be used.
5. In the plot of Z_L vs frequency of Table-5, we do not obtain a curve in lower frequencies, i.e, starting from 100Hz in our data, as a curve will be obtained if we have data for frequencies starting from 10Hz. Hence, we obtain a straight line when Z_L vs f is plotted.